

Student ID: \_\_\_\_\_

Name: \_\_\_\_\_

Assigned: March 29th

Due: April 5th at 11:59pm (Submit via the provided DEN link). No Late submissions.

**Notes:**

- This lab introduces you to FinFET circuit design as well as simulation with HSPICE.
- Your lab report must be **one pdf file**, which includes all the materials. Other file formats will not be graded.
- In this lab, please use viterbi-scf1.

## FinFET Circuit Design

### Double-Gate FinFET Basics

Fin-type field-effect transistors (FinFETs) are promising substitutes for bulk CMOS at the nanoscale. FinFETs are double-gate devices. The two gates of a FinFET can either be shorted for higher performance or independently controlled for lower leakage or reduced transistor count. This gives rise to a rich design space. This lab provides an introduction to various interesting FinFET logic design styles, and novel circuit designs. Figure 1 shows the shorted-gate (SG) FinFETs where the two gates are connected together, leading to a three-terminal device, and the independent-gate (IG) FinFETs, the top part of which is etched out, giving way to two independent gates. Because the two independent gates can be controlled separately, IG-mode FinFETs offer more design options.

 


Fig 1. (a) SG-mode FinFET; (b) IG-mode FinFET

In general, three modes of FinFET logic gates are logically obvious: (1) SG-mode, in which FinFET gates are tied together; (2) low-power (LP)-mode, in which the back-gate bias is tied to a reverse-bias voltage to reduce subthreshold leakage; and (3) IG-mode, in which independent signals drive the two device gates.

Figure 2 shows the implementation of a two-input NAND gate in each of the above modes. A hybrid IG/LP-mode NAND gate, which employs a combination of LP and IG modes is also presented. Similarly, other Boolean functions can be implemented in CMOS styles in each of the above-mentioned modes. ( $V_{hi}$  and  $V_{low}$  are the corresponding reverse-bias voltages.)

 


Fig 2. Different FinFET-based NAND gate designs

In this lab, you need to build basic gates for a given 7nm FinFET process, and compare the performance and power consumption of IG, LP, SG and IG/LP gate designs.

### What you are given

- hp7nfet.pm: n-type finfet model file from 7nm PTM high performance FinFET library
- hp7pfet.pm: p-type finfet model file from 7nm PTM high performance FinFET library

### Basic Setup for Hspice Simulation

- VDD=0.7V
- Input slope=10ps
- Gate length=11nm (it is still 7nm technology)  
.param lg=11n
- Upload the model files in the simulation folder and include the following lines:  
.include "hp7nfet.pm"  
.include "hp7pfet.pm"
- Define parameters for the number of fins:  
.param n\_fin = 1  
.param p\_fin = 1
- Example of drawing a single inverter:  
mn1 Z A Gnd Gnd nfet L=lg NFIN=n\_fin
- mp1 Z A Vdd Vdd pfet L=lg NFIN=p\_fin
- The back gate pin is the Body pin of the FinFET model
- Rise/Fall Delay: 0.5VDD of input to 0.5VDD of output
- Rise/Fall Time: 0.2VDD/0.8VDD of output to 0.8VDD/0.2VDD of output

### Tasks:

- Find the best number of fins for SG-mode 1X INV, NAND, NOR gates such that the rise and fall delays are balanced. Report the rise delay, fall delay, rise time, fall time, number of fins for n type

- and p type finfets for each gate, respectively.
- Find the rise delay, fall delay, rise time and fall time for 2X, 4X INV, NAND, NOR gates, respectively.
- Based on the 4 different 1X NAND gate designs in Figure 2, draw 4 1X NOR gate designs using the same number of fins. Compare the following items:
  1. rise delay, fall delay, rise time, fall time
  2. leakage power, switching power
  3. switching energy
- Design a 1-bit Full-Adder using any mode of FinFET.
  1. Perform functional test for all possible combinations of inputs  $(A, B, C) = (0,0,0) \sim (1,1,1)$  and report the output.
  2. Report Rise/Fall Delay.

### Hints

You may write multiple hspice files and a perl or python script to assist the simulation process. It is possible that the back gate won't affect the performance significantly.

### What you need to submit

#### One PDF report which contains:

- 1) For each task, you need to have screenshot of ONE hspice file (though you have multiple hspice files)
- 2) Perl/python script screenshot if you have any
- 3) Results of each task

### Reference:

Mishra, Prateek, Anish Muttreja, and Niraj K. Jha. "Finfet circuit design." Nanoelectronic Circuit Design. Springer New York, 2011. 23-54.

PTM library available [online]: <http://ptm.asu.edu/>

## PTM FinFET DRAM

### Hspice Simulation

- 1) Implement a one-bit 1T DRAM cell in Hspice initially with  $\text{Fin}\#=1$  and  $C=1\text{fF}$  using the PTM FinFET CMOS technology and the circuit setup shown in Figure 1.
- 2) Do transient analysis for a time duration  $T$ .  $T$  should be selected long enough to see  $V_C$  discharging to  $V_{DD}/2$  (due to leakage). The time it takes for  $V_C$  to discharge from  $V_{DD}$  to  $V_{DD}/2$  is referred to as Refresh Time Limit (R.T.L.). Use the trig-targ command in Hspice to calculate the R.T.L. Also use the AVG command to find the average capacitance current ( $I_{\text{avg}}$ ). Finally, use the AVG command to measure the average power dissipated by the capacitance ( $P_{\text{avg}}$ ).

 


Figure 1: Circuit setup

### Python scripting and Matlab analysis

- 3) Sweep Fin# between 1 and 5 and sweep C logarithmically between 1fF and 50pF for 11 different values (1f, (50,000)<sup>(0.1)</sup>f, (50,000)<sup>(0.2)</sup>f, ..., (50,000)f). Calculate the R.T.L., I<sub>avg</sub>, P<sub>avg</sub> for each combination of C-W values and print the results in a text file named **dram.txt**. Note that the larger is C, the longer is T needed to measure R.T.L.
- 4) Write a Matlab m-file, **analysis.m**, to read the dram.txt file and plot the 3D graphs of
  - i. R.T.L. vs. (C, Fin#)
  - ii. I<sub>avg</sub> vs. (C, Fin#)
  - iii. P<sub>avg</sub> vs. (C, Fin#)
- 5) In the **eval.m** calculate the following statistics: min, max, standard deviation, and average of
  - i. R.T.L.
  - ii. I<sub>avg</sub>
  - iii. P<sub>avg</sub>

### Implementation Details:

- Hspice does not have a GUI and we need other software to visualize the output waveforms. In this lab, we use Wave Viewer.
- Run the hspice file using this command (filename.sp is the name of the hspice file you created): hspice filename.sp
- You should see no error after running hspice (warnings are fine).
- A lot of output files will be created by hspice. We are interested in \*.tr0 (transient analysis output) and \*.mt0 (measurements output).
- You can download Matlab to your laptop from ITS: <http://www.usc.edu/its/software/>
- Useful commands for Matlab:
 

```
Matlab -nojvm
help max, min...
Comment %
Example:
wset=load('/home/scf-16/yue/EE577a/dram.txt');
c=[1:1:10]; %x-array: one-dimensional
d=[1:1:10]; %y-array: one-dimensional
h=c'*d; %z-matrix: two-dimensional
surf(c,d,h) % Plot 3D graph
```

### Report

- 1) The spice deck
- 2) Perl/Python script
- 3) dram.txt

- 4) analysis.m
- 5) 3D graphs of R.T.L.,  $I_{avg}$  and  $P_{avg}$
- 6) Calculated statistic values